



DA DRONACHARYA ACADEMY
Subject Wise TEST
BRANCH- ELECTRICAL ENGINEERING
Subject - Network Theory

Maximum marks :- 20

Time :- 30 min

Name :-

Date:-

Marks Obtained :-

INSTRUCTIONS TO STUDENTS


- 1. Write your name on your test booklet.**
- 2. Rough work to be done in the test booklet only.**
- 3. Each question carries 1.0 marks. For each correct answer 1.0 mark shall be awarded. Question not attempted shall be ignored. For wrong answer 0.25 marks will be deducted. There is negative marking in the test.**

Use of electronics/manual calculator and any electronics equipment like mobile phone etc. is not allowed.

1. **Superposition theorem is valid for which of the following circuit elements?**
- (a) Non-linear elements
 - (b) Passive elements
 - (c) Linear bilateral elements
 - (d) Resistive elements


2. **Thevenin's theorem converts a circuit to an equivalent form consisting of**
- (a) a current source and a series resistance
 - (b) a voltage source and a parallel resistance
 - (c) a voltage source and a series resistance
 - (d) a current source and a parallel resistance

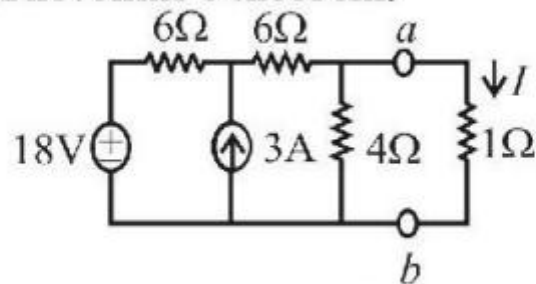3. **For the circuit shown here find the current I using Thevenin's theorem.**



- (a) 1.50 A
- (b) 1.75 A
- (c) 2.25 A
- (d) 1.25 A

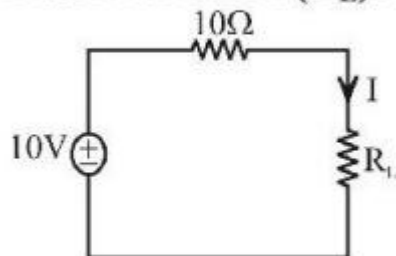4. **Find the maximum power transferred to the load resistance (R_L).**




- (a) 1.0W
- (b) 2.5W
- (c) 6.0W
- (d) 4.0W

12. **The Superposition theorem is used when the circuit contains :**
- (a) A single voltage source
 - (b) active elements only
 - (c) a number of voltage sources
 - (d) passive elements only

13. **Which one of the expression satisfies the condition of maximum power transfer theorem?**
- (a) $Z_L = Z_S^*$
 - (b) $Z_L = R_L$
 - (c) $Z_L = 2Z_S$
 - (d) $X_L = R_L$

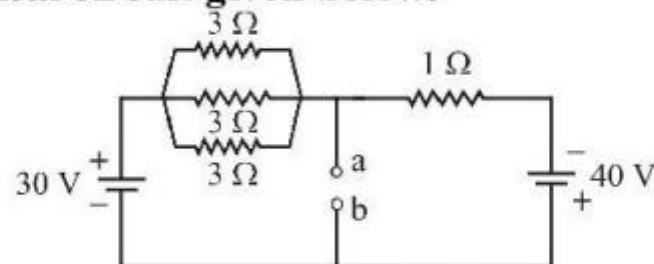14. **Determining the Thevenin's equivalent resistance (in ohms) across the terminal a and b for the electrical circuit given below.**



- (a) 1
 - (b) 0.5
 - (c) 0.3
 - (d) 0.2
15. **Which of the following statement is CORRECT?**
- (a) Superposition theorem is applicable to only those circuits that only have active elements.
 - (b) Superposition theorem is applicable to only those circuits that only have passive elements.
 - (c) Superposition theorem is applicable to only those circuits that only have linear bilateral elements.
 - (d) Superposition theorem is applicable to only those circuits that only have non-linear bilateral elements.